

---

# Explanation of S11 and S21 in Spice Simulation

KS Kelvin Kelvin Leung  
Created on 4-26-2023  
Last Updated on 8-6-2025

---

# Basic of S11 and S21

- Definition of S11 and S21

- $S_{11} = \frac{v_{rev,port1}}{v_{fwd,port1}} = \sqrt{\frac{P_{rev,port1}}{P_{fwd,port1}}}$ 
  - Given  $v_{rev,port2} = 0V$  (  $p_{rev,port2} = 0W$  )
- $S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \sqrt{\frac{P_{fwd,port2}}{P_{fwd,port1}}}$ 
  - Given  $v_{rev,port2} = 0V$  (  $p_{rev,port2} = 0W$  )

- Remark

- Measurable voltage (  $v_{rf}$  ) is summation of forward and reverse voltage
  - $v_{rf} = v_{fwd} + v_{rev}$



# How to Simulate S21 in Spice with AC Sweep

- Refer to S21 Definition


- $$S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \sqrt{\frac{P_{fwd,port2}}{P_{fwd,port1}}}$$
  - Given  $v_{rev,port2} = 0$  ( $p_{rev,port2} = 0$ )

- Simulation Idea

- As no reflection at port 2, system must be terminated by characteristic impedance (50 Ohms)
- As no reflection, direct voltage ( $v_{rf,port2}$ ) measurement at system output equal  $v_{fwd,port2}$ 
  - $v_{rf} = v_{fwd} + v_{rev}$ , if  $v_{rev} = 0$ ,  $v_{rf} = v_{fwd}$
- If Port 1 is setup to give a forward 1V voltage (i.e.  $v_{fwd,port1} = 1V$ ), AC Sweep voltage at port 2 is S21 as
  - $S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \frac{v_{rf,port2}}{1}$
- By Port 1 as a 2V voltage source with 50 ohms source impedance, it can guarantee  $v_{fwd,port1} = 1V$  in regardless of port 1 loading condition




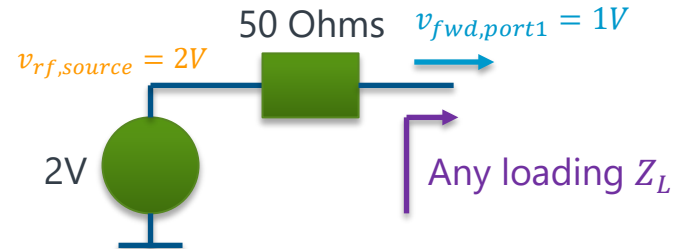**Port 1 guarantee to generate 1V forward voltage**



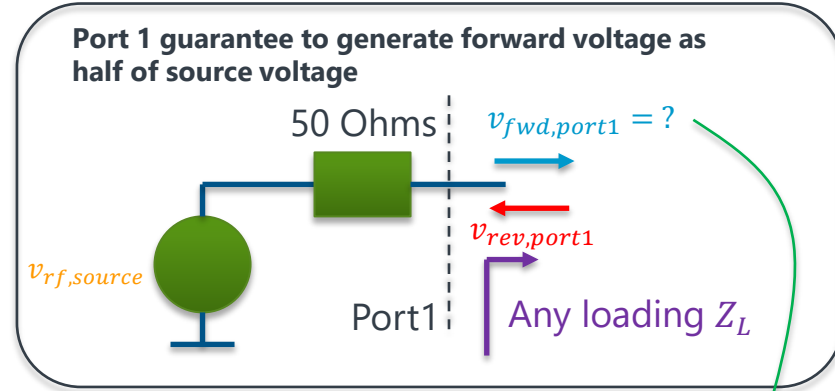
# How to Simulate S21 in Spice with AC Sweep

- Why this circuit must generate a forward voltage equal half of source voltage
  - In theory, forward voltage is the voltage wave that travels forward and terminates into the characteristic impedance  $Z_0$  (50 ohms)
  - For a circuit with a voltage source in series with a 50-ohm resistor, regardless of the loading condition, if we only need to know the forward voltage, we can assume we couple the forward wave and feed it into the 50-ohm impedance
  - The forward-only circuit now becomes a simple voltage divider, and the forward voltage must equal half of the source voltage  $v_{fwd,port1} = \frac{v_{rf,source}}{2}$
  - Therefore, the advantage of having a 50-ohm in series with the source is that it terminates the reverse wave and forced forward voltage to equal half of the source voltage
  - This is also why signal generators are designed to have a source impedance equal to the characteristic impedance  $Z_0$ , as their voltage or power setpoint can always be related to the forward voltage or forward power with only a scaling factor



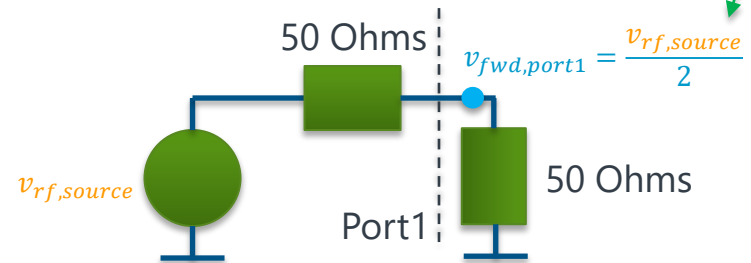
Couple forward wave and feed into 50 ohms load




# How to Simulate S11 in Spice with AC Sweep

- $S_{11}$  rely on conversion from  $Z_{11}$ 
  - $Z_{11}$  is impedance measured from port 1 with port 2 terminated at 50ohms
    - If no output from circuit, port 2 not exist and both forward and reverse at port 2 must be 0
  - $Z_{11}$  is a direct measurable parameter in AC Sweep by  $Z_{11} = \frac{v_{rf,source}}{i_{rf,source}}$
  - Conversion is  $S_{11} = \frac{Z_{11} - Z_0}{Z_{11} + Z_0}$
- A single circuit in Spice to measure both S11 and S21
  - It is possible to use S21 port 1 circuit but measure  $v_{rf}$  and  $i_{rf}$  after source impedance and calculate  $Z_{11} = \frac{v_{rf,x}}{i_{rf,x}}$

Port 1 Circuit to Measure Z11

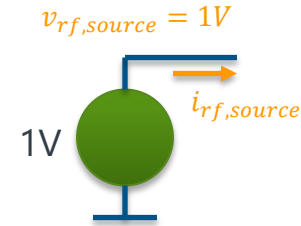

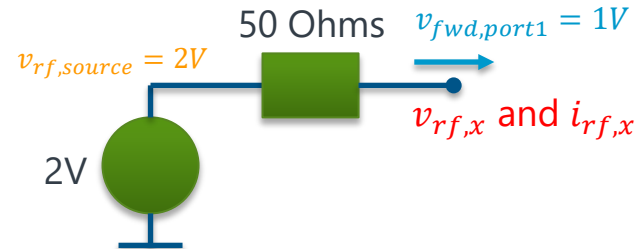
Single Circuit in Spice to Measure S11 and S21




## Spice Simulation for S11 and S21

# LTSpice Simulation for $Z_{11}$ and $S_{21}$ : LTSpice\_Sparam\_Simulation.asc

## Schematic

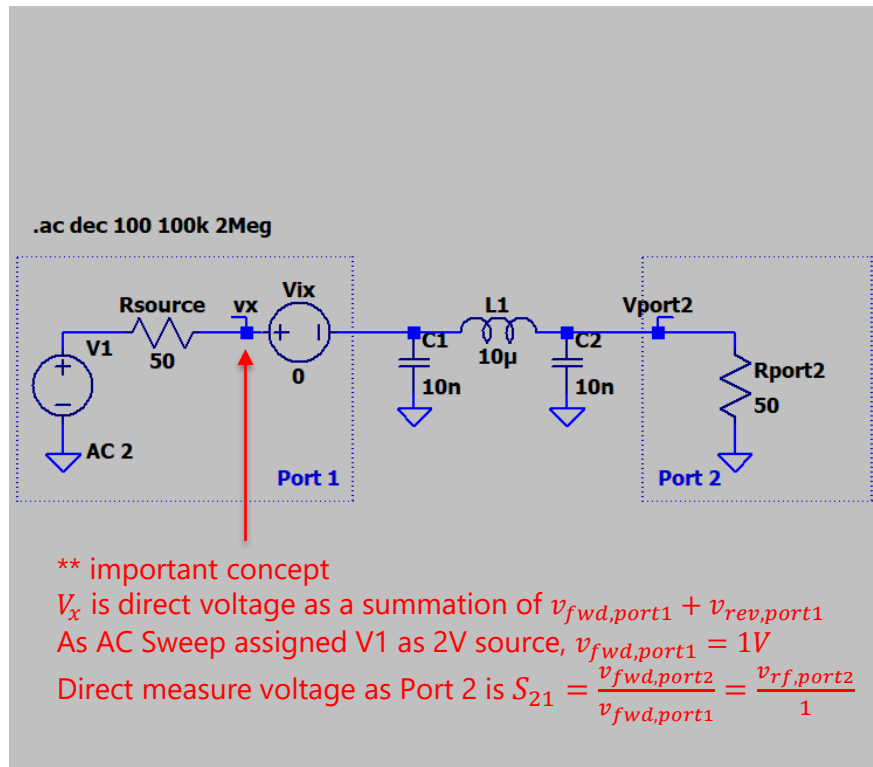


## Simulation Result

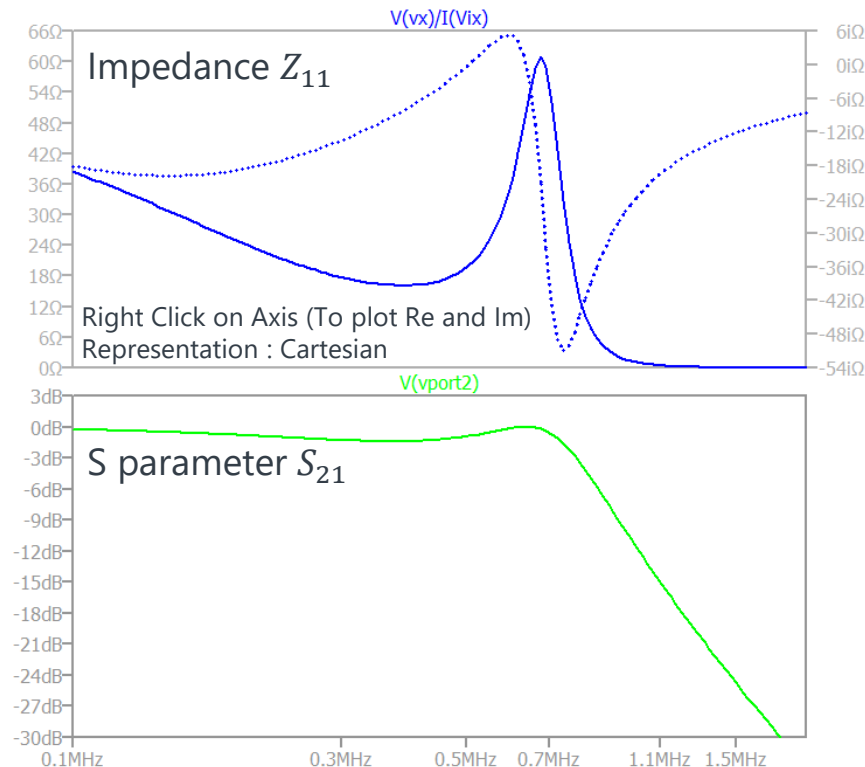

# QSpice Simulation for $S_{11}$ and $S_{21}$ : QSpice\_Sparam\_Simulation.asc

## Schematic

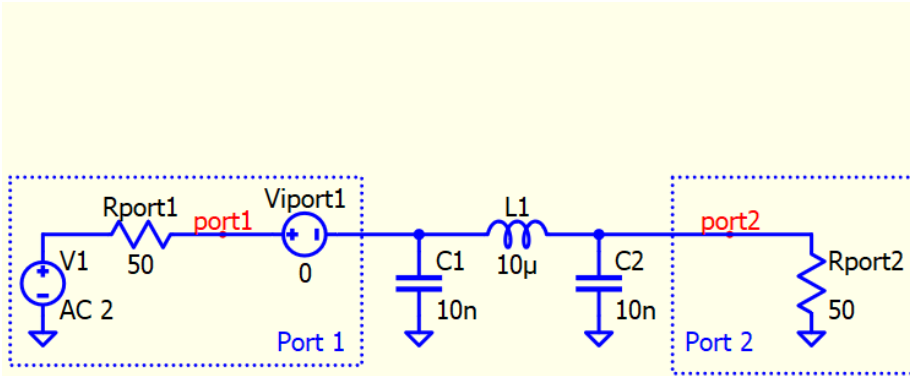


```
.param Zo=50
.func Z11() V(port1)/I(Viport1)
.func S11() (Z11()-Zo)/(Z11()+Zo)
.func S21() V(port2)
.ac dec 100 100K 2Meg
.plot S21()
.plot S11()
```

**\*\* important concept**

$V(\text{port1})$  is direct voltage as a summation of  $v_{fwd, \text{port1}} + v_{rev, \text{port1}}$   
As AC Sweep assigned V1 as 2V source,  $v_{fwd, \text{port1}} = 1V$

Direct measure voltage as Port 2 is  $S_{21} = \frac{v_{fwd, \text{port2}}}{v_{fwd, \text{port1}}} = \frac{v_{rf, \text{port2}}}{1}$

## Simulation Results

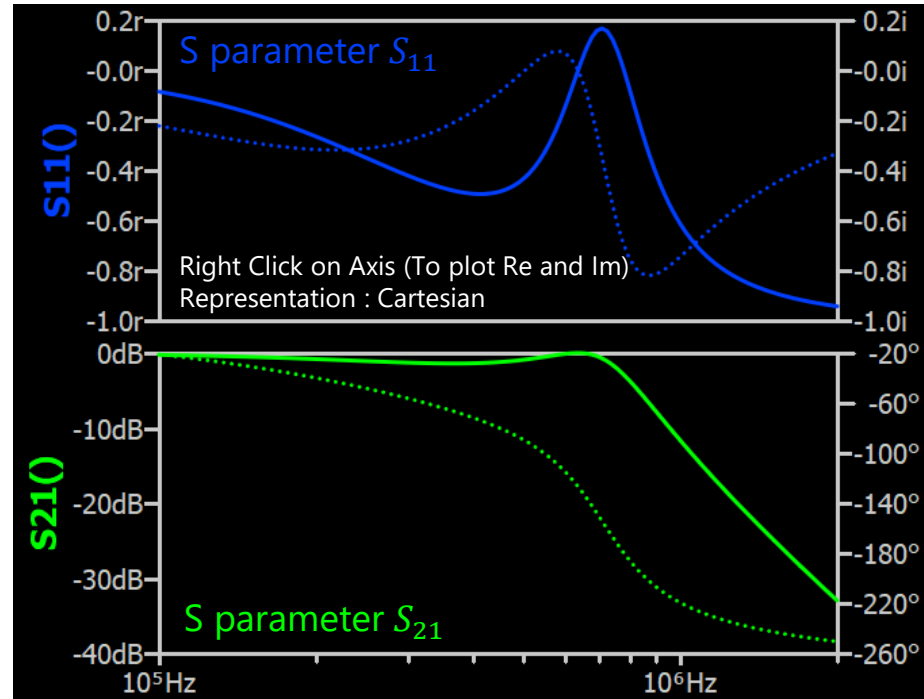




# QSpice Simulation for $S_{11}$ and $S_{21}$ : QSpice\_Sparam\_Simulation.asc
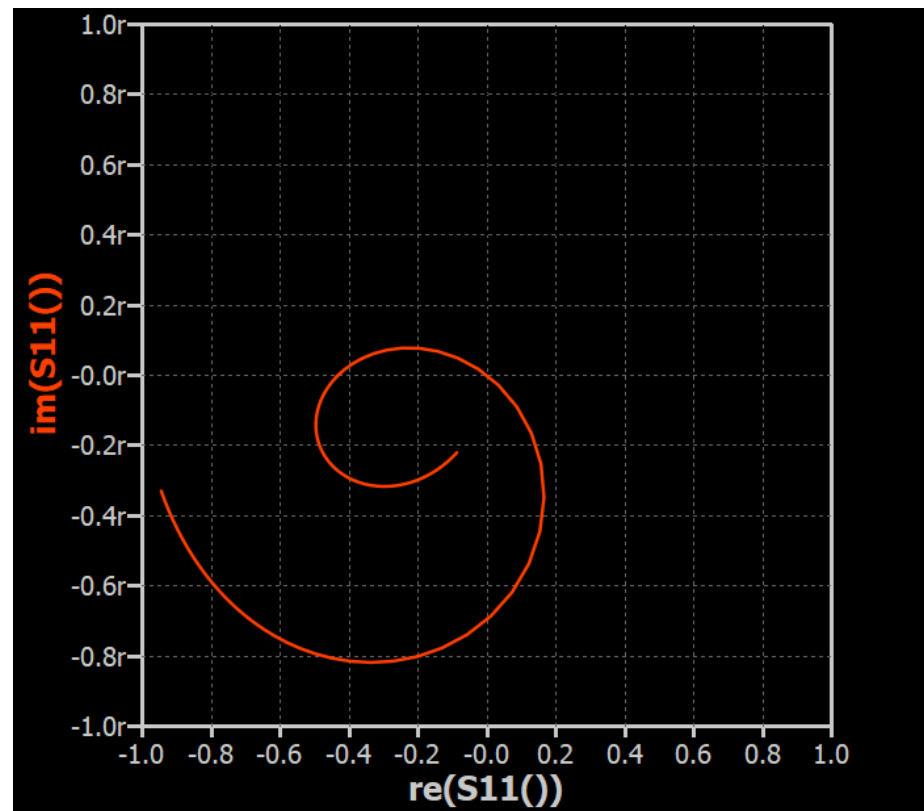
## How to Plot $S_{11}$ in QSpice

- Plot  $S_{11}$ 
  - Qspice supports Catesian Representation,  $S_{11}$  can be plotted in a X-Y plot format
  - Add plot expression :  $\text{im}(S_{11}())$
  - Right Click left y-axis
    - change to Cartesian Representation
    - Change range to Top=1r, Tick=0.2r, Bottom=-1r
  - Right Click right y-axis
    - select No Imaginary
  - Right Click x-axis
    - Change Quantity Plotted to  $\text{re}(S_{11}())$
    - Dis-select Logarithmic
    - Change range to Left=-1, Tick=0.2, Right=1



# QSpice Simulation for $S_{11}$ and $S_{21}$ : QSpice\_Sparam\_Simulation.asc

## $S_{11}()$ in SmithChart Representation

\*\* User can also post-processing data to plot in SmithChart

Method to plot  $S_{11}$  in Microsoft Excel

[1] In Qspice Waveform Viewer, File > Export, Select to export  $S_{11}()$  in csv format. Exported  $S_{11}$  is in format of  $[re(S_{11}), im(S_{11})]$

[2] Rename .csv to .txt, use Excel to import this .txt. In Import Wizard, it will ask for delimiters, select both "Tab" and "Comma"

[3] Use X-Y Scatter plot to plot with x-axis  $Re(S_{11})$  and y-axis  $Im(S_{11})$

Text Import Wizard - Step 2 of 3

This screen lets you set the delimiters your data contains. You can see how your text is affected in the preview below.

Delimiters

☒ Tab

☐ Semicolon

☒ Comma

☐ Space

☐ Other:

☐ Treat consecutive delimiters as one


Text qualifier: "

Data preview

Frequency	$S_{11}()$	
100000	-0.085738537031553	-0.222103470085669
100300.022396366	-0.0862069839856257	-0.222604649083563
100600.944927116	-0.0866768363854754	-0.223107331730697
100902.770292853	-0.0871480984477546	-0.223611522538355
101205.501202285	-0.0876207744017664	-0.224117226031357


Cancel < Back Next > Finish

Frequency	$S_{11}()$	Real	Imag
100000	-0.08574	-0.2221	
100300	-0.08621	-0.2226	
100600.9	-0.08668	-0.22311	
100902.8	-0.08715	-0.22361	
101205.5	-0.08762	-0.22412	
101509.1	-0.08809	-0.22462	
101813.7	-0.08857	-0.22513	
102119.2	-0.08905	-0.22564	
102425.5	-0.08953	-0.22615	
102732.8	-0.09001	-0.22665	
103041.1	-0.0905	-0.22716	
103350.2	-0.09099	-0.22767	
103660.3	-0.09148	-0.22817	
103971.3	-0.09197	-0.22868	
104283.2	-0.09247	-0.22919	
104596.1	-0.09296	-0.2297	
104909.9	-0.09346	-0.23021	
105224.7	-0.09397	-0.23072	
105540.4	-0.09448	-0.23122	

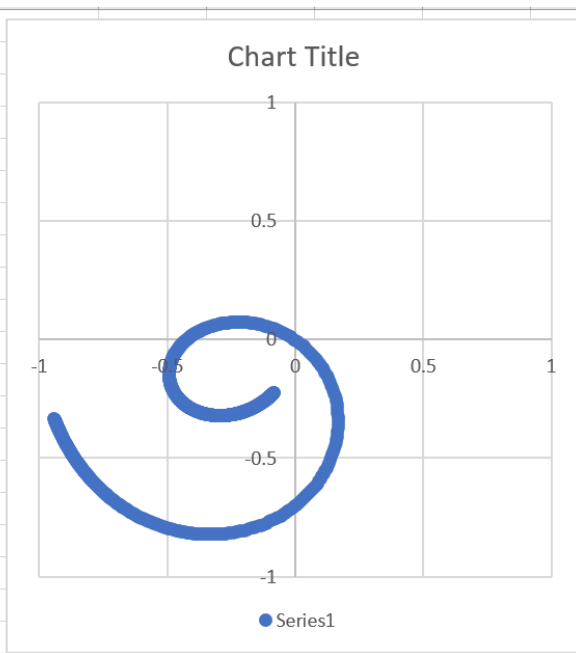


# SimNEC Simulation for $S_{11}$ and $S_{21}$ : SimNEC\_Sparam\_Simulation.ssn

## Schematic

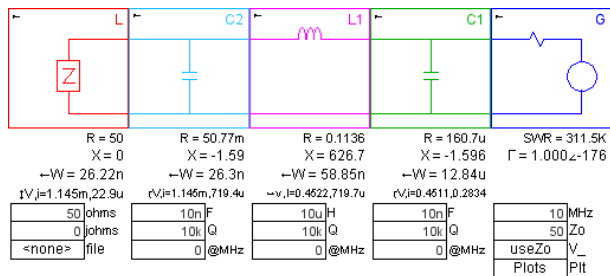

## SmithChart S11

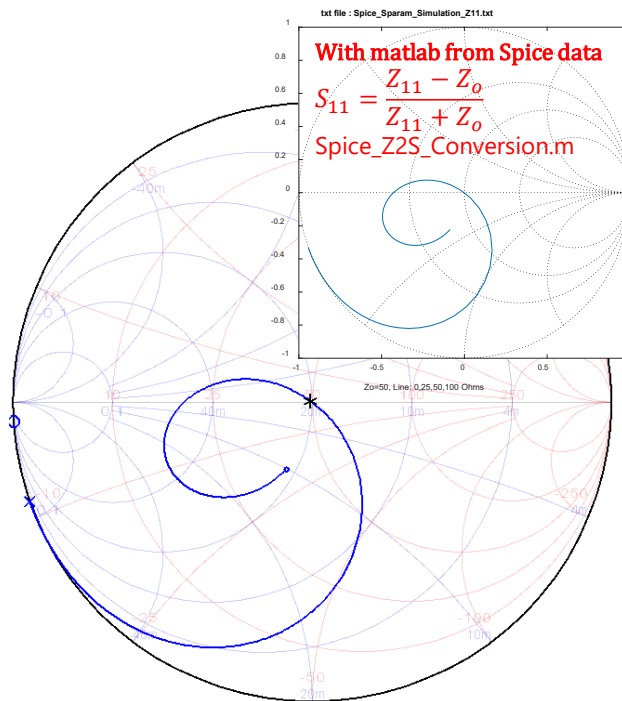

## Gain Chart S21

