
Spice S-parameter Measurement with MicroSim AppNote Method


KS Kelvin Kelvin Leung
Created on 12-9-2023

S-Parameters Measurement Circuit


- S-Parameters Measurement Circuit
 - Reference : MicroSim Application Notes
Version 8 June-1997
 - Section : Create S-Parameter Subcircuits for
Microwave and RF Applications

Definition of S11 and S21

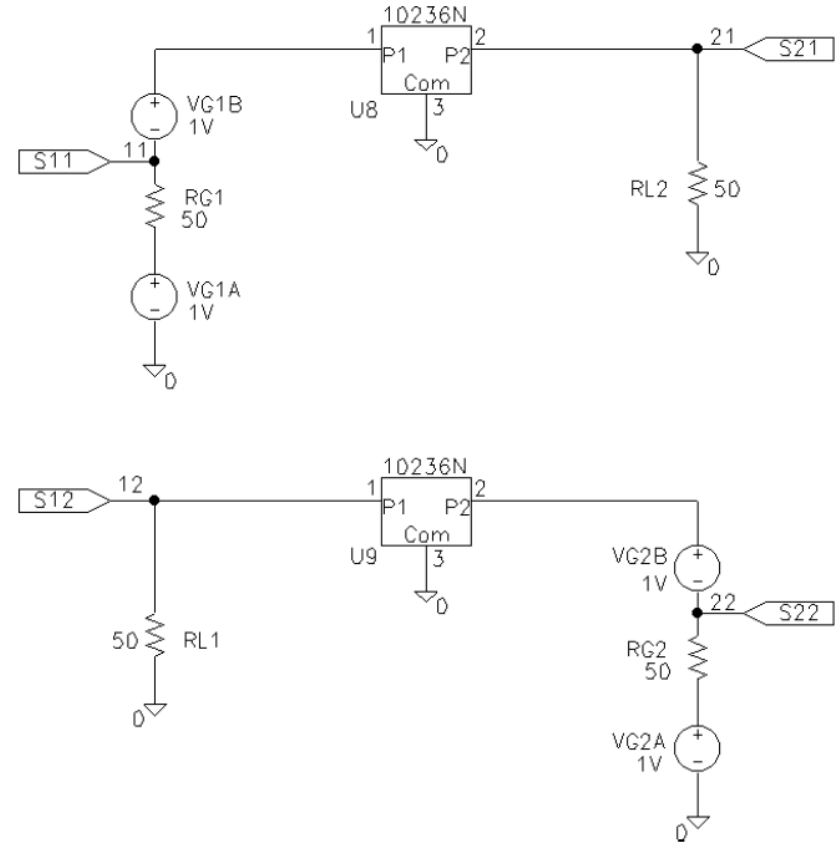- $S_{11} = \frac{v_{rev,port1}}{v_{fwd,port1}} = \sqrt{\frac{P_{rev,port1}}{P_{fwd,port1}}}$
 - Given $v_{rev,port2} = 0V$ ($p_{rev,port2} = 0W$)
- $S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \sqrt{\frac{P_{fwd,port2}}{P_{fwd,port1}}}$
 - Given $v_{rev,port2} = 0V$ ($p_{rev,port2} = 0W$)
- Measurable voltage (v_{rf}) is summation
of forward and reverse voltage
 - $v_{rf} = v_{fwd} + v_{rev}$



S-Parameters Measurement Circuit

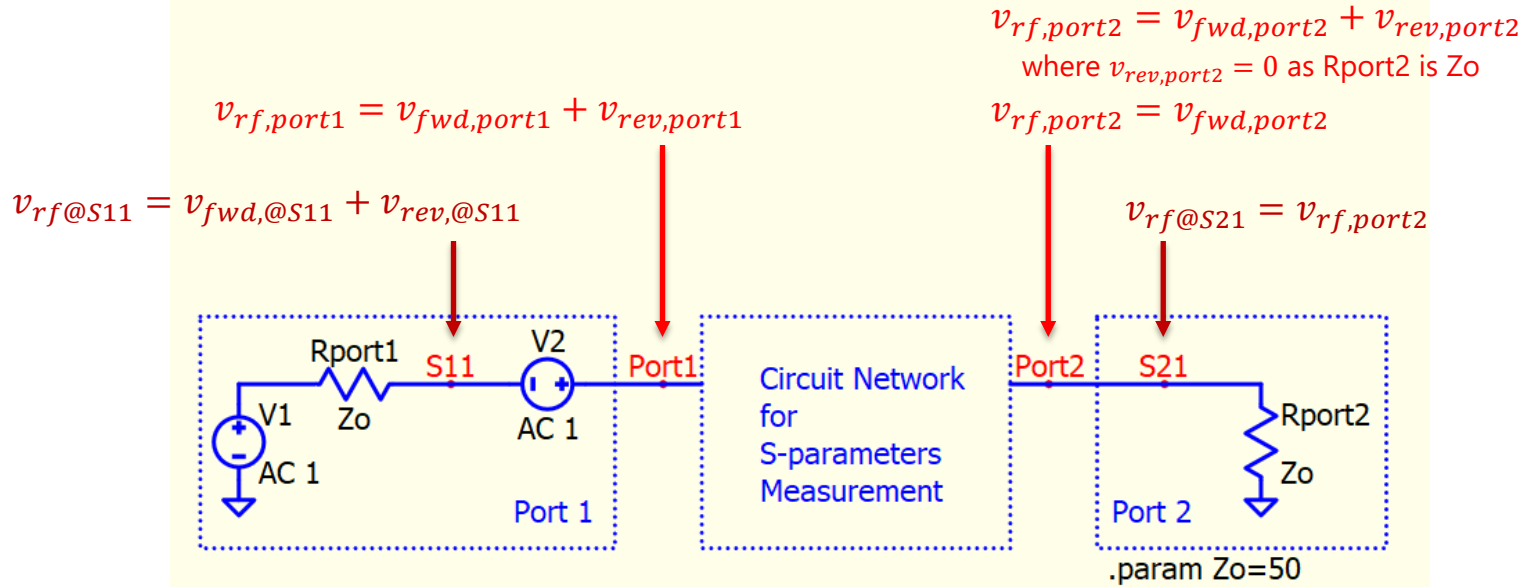

Explanation of S21

• Forward voltage @ Port1

- To measure forward voltage @ Port1, break connection and connect a terminal impedance equal characteristic impedance (Z_o)

- $v_{rev,port1} = 0$
- Kirchhoff's voltage law



$$v_{fwd,port1} = \frac{Z_o}{Z_o + Z_o} (1 + 1) = 1$$

• Forward voltage @ Port2

- As Port2 is terminated with Z_o , $v_{rev,port2} = 0$
- $v_{rf,port2} = v_{fwd,port2} + v_{rev,port2} = v_{fwd,port2}$
- $v_{fwd,port2} = v_{rf,port2} = v_{rf,@S21}$

• By $S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \frac{v_{rf,@S21}}{1} = v_{rf,@S21}$

- Therefore, $S21 = V(S21)$

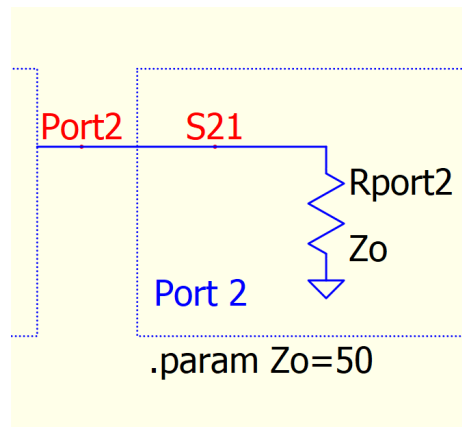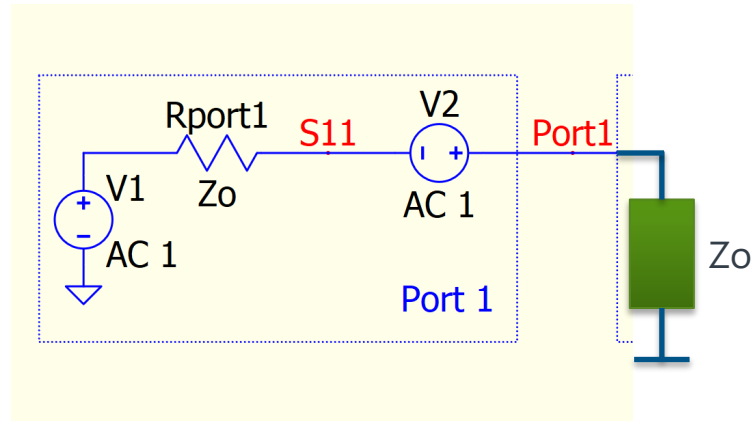

Explanation of S11

- Forward voltage @ Port1

- To measure forward voltage @ Port1, break connection and connect a terminal impedance equal characteristic impedance (Z_o)

- $v_{rev,port1} = 0$

- $v_{fwd,port1} = \frac{Z_o}{Z_o + Z_o} (1 + 1) = 1$

- Kirchhoff's voltage law

$$v_{fwd,@S11} = -1 + v_{fwd,port1} = 0$$

- Reverse voltage @ Port1

- $v_{rf,port1} = v_{fwd,port1} + v_{rev,port1}$

$$v_{rf,port1} = 1 + v_{rev,port1}$$

- Kirchhoff's voltage law


$$v_{rf,@S11} = -1 + v_{rf,port1}$$

$$v_{rf,@S11} = -1 + 1 + v_{rev,port1} = v_{rev,port1}$$

- By $S_{11} = \frac{v_{rev,port1}}{v_{fwd,port1}} = \frac{v_{rev,port1}}{1} = v_{rf,@S11}$

- Therefore, $S_{11} = V(S_{11})$

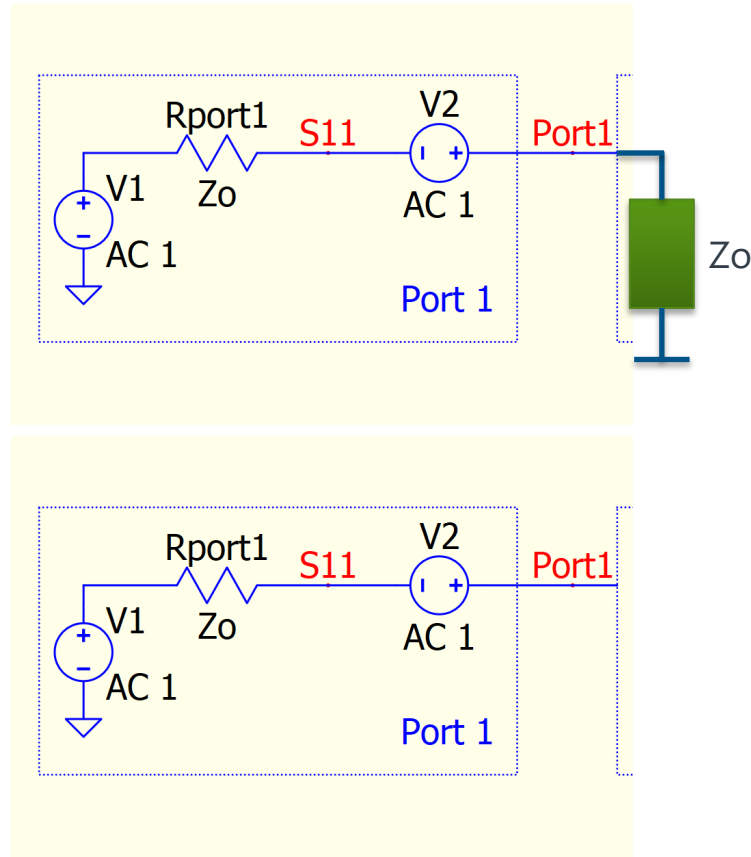
- ** The beauty of this method is that, $V(S_{11})$ measure 0V forward voltage and only measure reverse voltage.




QSpice Simulation for S_{11} and S_{21} :

QSpice Sparam Simulation MicroSim.qsch

Schematic

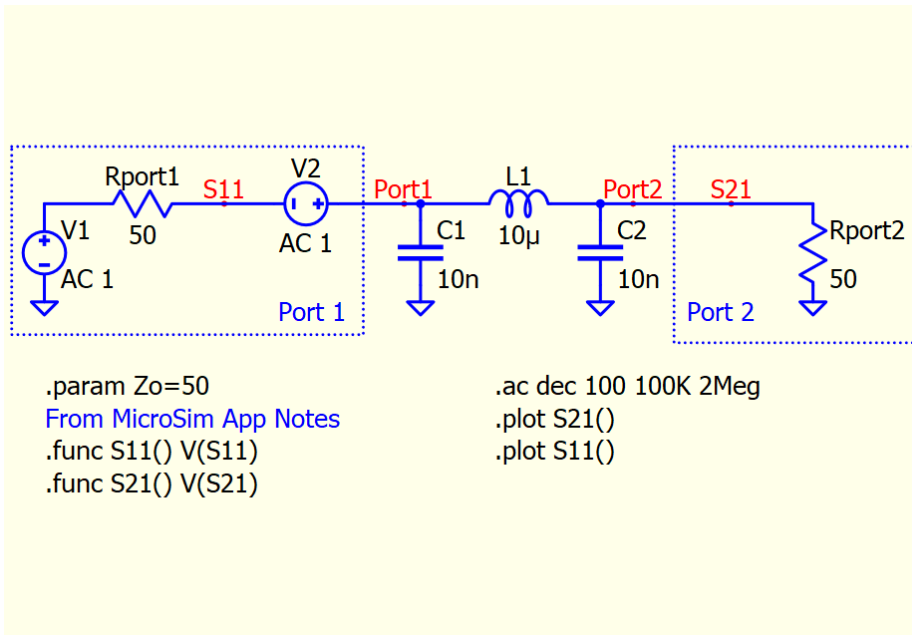

Simulation Results

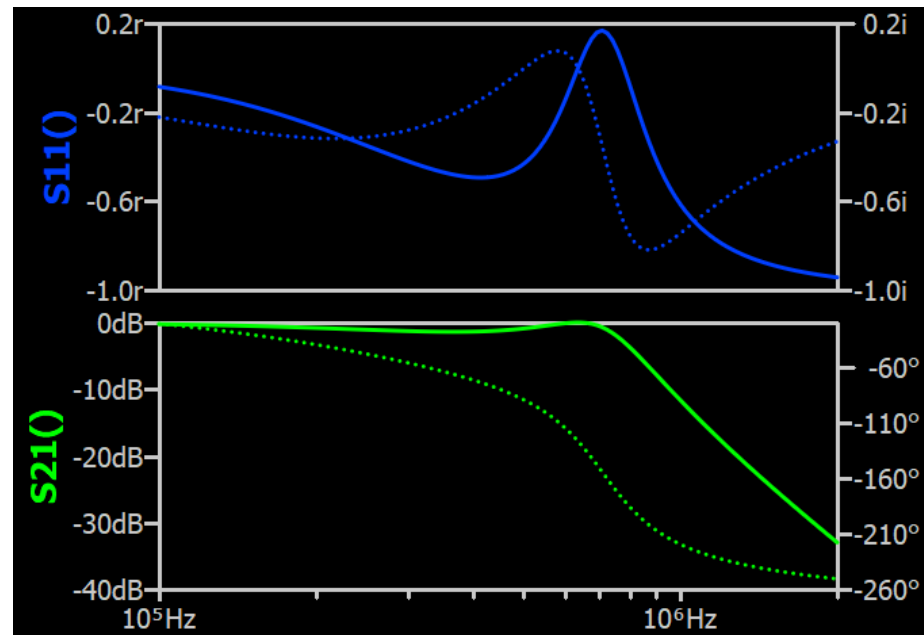

Plot S11 into SmithChart Range

- Plot S11 into SmithChart Range
 - Method
 - Plot S11 with y-axis as $\text{imag}(S11)$ and x-axis as $\text{real}(S11)$, and plot have to be Cartesian representation
 - Y-Axis (Left)
 - Change Y expression to : $\text{im}(S11())$
 - Change Representation from Polar to Catesian
 - Change Range from -1 (bottom) to +1 (top)
 - Y-Axis (Right)
 - X-Axis
 - Change Quantity Plotted to : $\text{re}(S11())$
 - Change Range from -1 to 1
 - Disable "Logarithmic"

