

---

# Qspice KSKelvin Symbol Explanation

KSKelvin Kelvin Leung

Created on 9-3-2023  
Last Updated on 12-28-2023

---

# Ideal Opamp

Qspice : Opamp\_Ideal.qsym

# Ideal Operation Amplifier - Overview

Qspice : ComptrOD\_Ideal.qsym

- Ideal Opamp Sub-Circuit
  - opamp.sub in LTspice library

\* Copyright © Linear Technology Corp. 1998, 1999, 2000. All rights reserved.

```
.subckt opamp 1 2 3
```

```
G1 0 3 2 1 {Aol}
```

```
R3 3 0 1.
```

```
C3 3 0 {Aol/GBW/6.28318530717959}
```


```
.ends opamp
```

- Opamp equivalent formula

$$V_{output} = Z(R_3, C_3) \times Aol \times I_{G1}$$

$$V_{output} = (R_3 // \frac{1}{j\omega C_3}) \times Aol \times (V_p - V_n)$$

Opamp.sub Equivalent Schematic

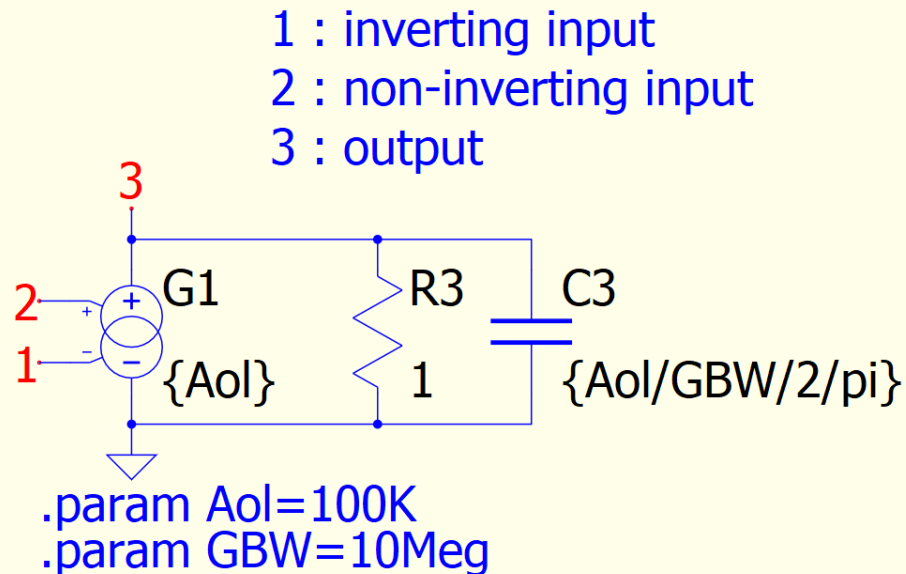

# Ideal Operation Amplifier – Parameters of Symbol

Qspice : ComptrOD\_Ideal.qsym

Method #1

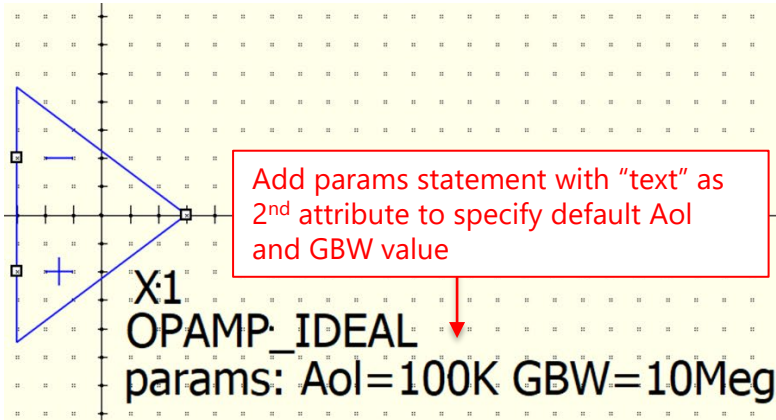


Diagram of an ideal op-amp symbol (X1) with parameters: **OPAMP\_IDEAL** and **params: Aol=100K GBW=10Meg**. A red box highlights the text "Add params statement with 'text' as 2nd attribute to specify default Aol and GBW value".

**Symbol Properties**

Application	
[Icons]	
Basics	
Symbol Type	X
Description	Ideal Opamp
Allow Shorted Pins	False
Library File	subckt opamp_ideal 1 2 3 nG1 ...
String Attributes	
Text Order	Invis. Content
Name:	X1
1st attribute	OPAMP_IDEAL
2nd attribute	params: Aol=100K GBW=10Meg
Pin Nets	
Pin Name	Invis. Net
1	
2	
3	

Right click on 2nd attribute and make parameters attribute invisible in symbol if needs

Method #2

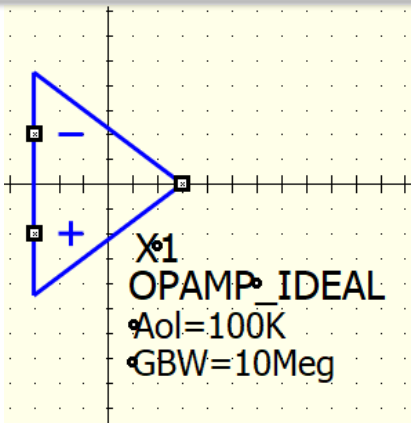


Diagram of an ideal op-amp symbol (X1) with parameters: **OPAMP\_IDEAL** and **Aol=100K GBW=10Meg**.



**Symbol Properties**

Application	
[Icons]	
Basics	
Symbol Type	X
Description	Ideal Opamp
Allow Shorted Pins	False
Library File	subckt opamp_ideal 1 2 3 nG1 0 3 2 1
String Attributes	
Text Order	Invis. Content
Name:	X1
1st attribute	OPAMP_IDEAL
2nd attribute	Aol=100K
3rd attribute	GBW=10Meg



Add text for extra attribute Aol and GBW

# Ideal Operation Amplifier - Simulation Example

Parent - opamp\_ideal (.ac).qsch

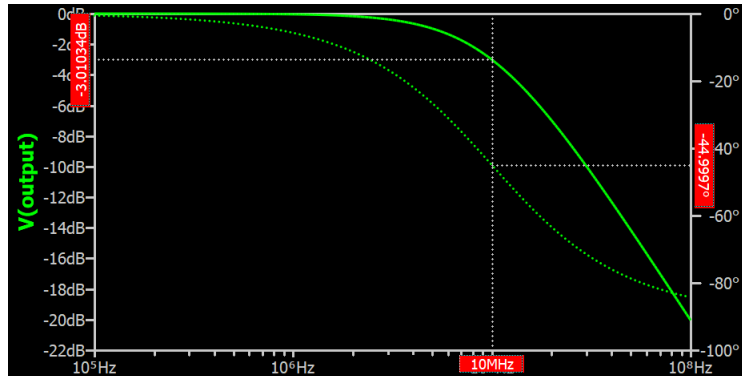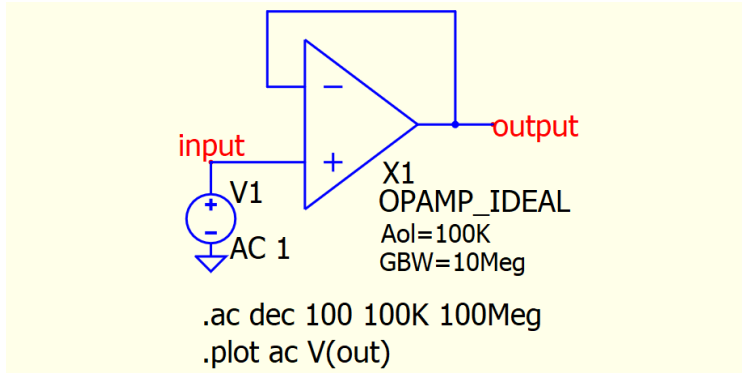

Parent - opamp\_ideal (.tran).qsch

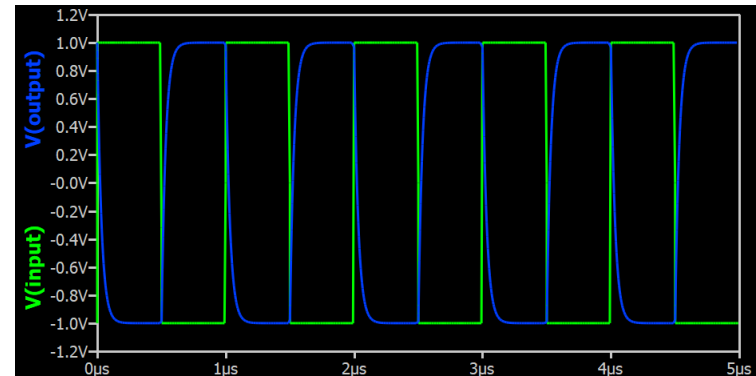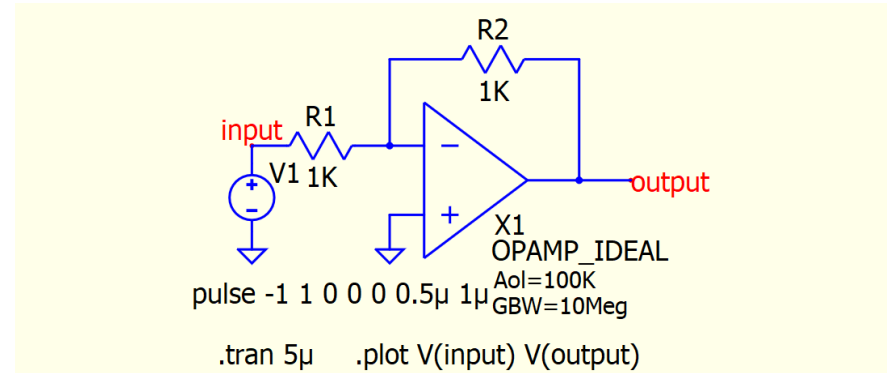

# Ideal Comparator

Qspice : Compr\_Ideal.qsym


Qspice : ComprOD\_Ideal.qsym

Qspice : Compr\_Ideal\_Supply.qsym

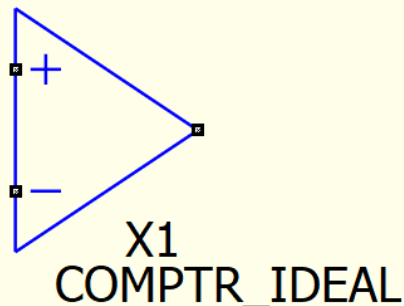
# 3 type of Ideal Comparators Overview

Qspice : Comptr\_Ideal.qsym / Comptr\_Ideal\_Supply.qsym / ComptrOD\_Ideal.qsym





Ideal Comparator (Output 0/1)  
Comptr\_Ideal.qsym



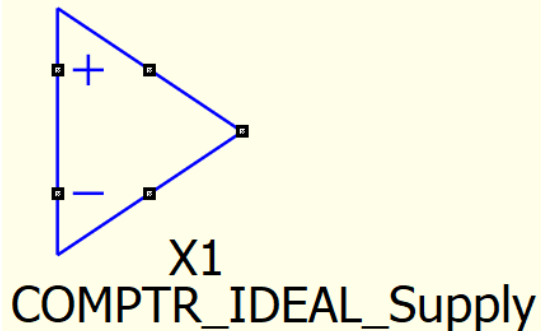Ideal Comparator (Vdd/Vss)  
Comptr\_Ideal\_Supply.qsym



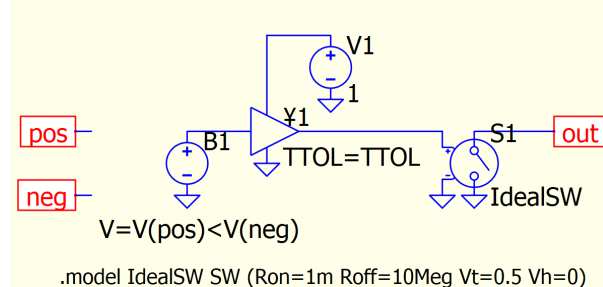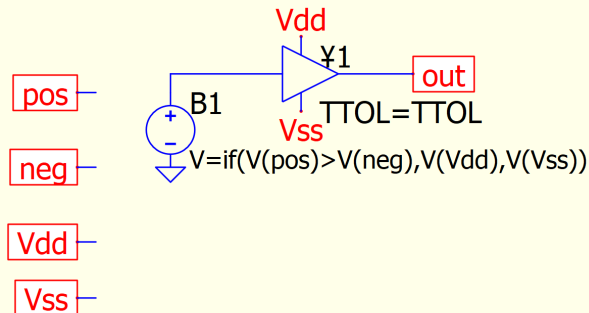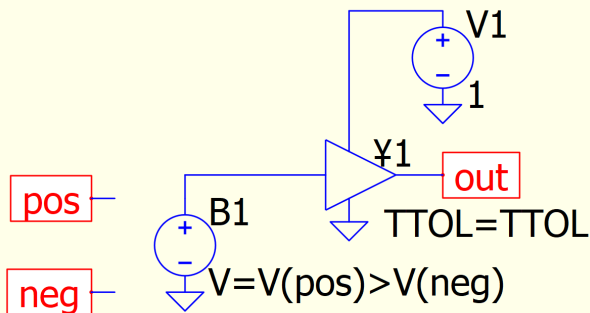
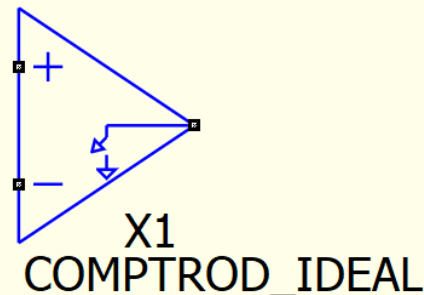
Ideal Comparator (Open Drain)  
ComptrOD\_Ideal.qsym



.model IdealSW SW (Ron=1m Roff=10Meg Vt=0.5 Vh=0)

# 3 type of Ideal Comparators – Simulation Results

Qspice : Parent - Comparator.qsch

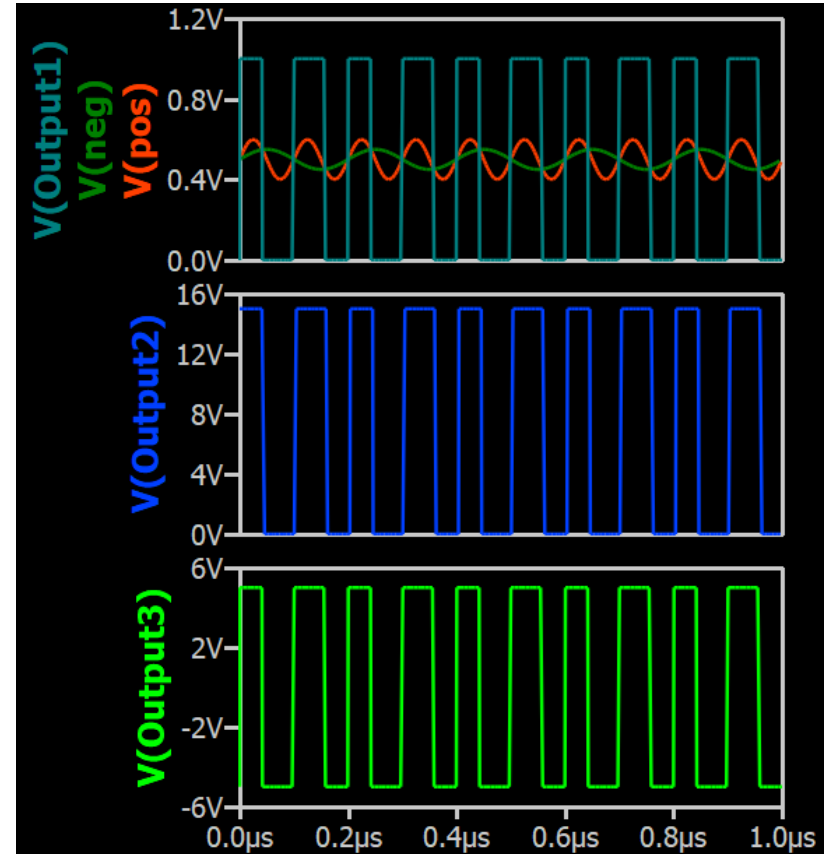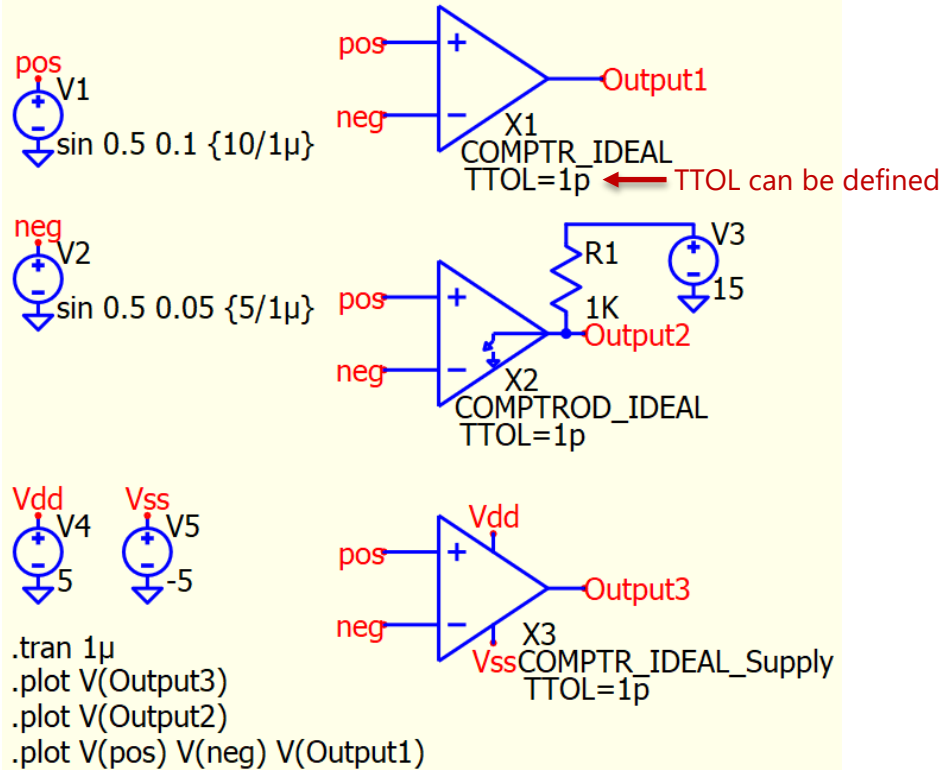



# Control System

## Gain, Different, PID and Signal Limiter

Qspice : Gain.qsym

Qspice : Different.qsym

Qspice : PID.qsym


Qspice : Signal\_Limiter.qsym

# Gain and Different

Qspice : Gain.qsym / Difference.qsym



- Gain

- $V_{out} = A_v \times V_{input}$

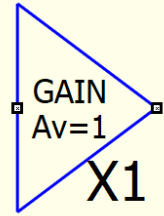


- Difference

- $V_{out} = V_+ - V_-$

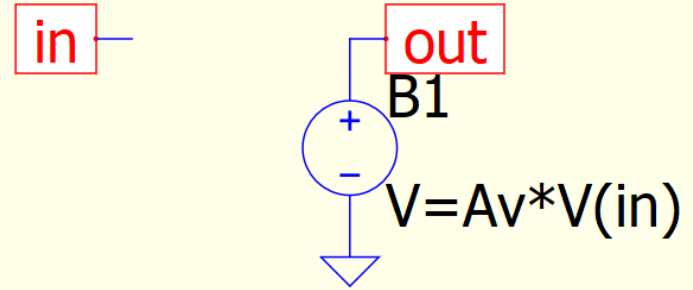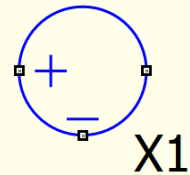

.param Av=1

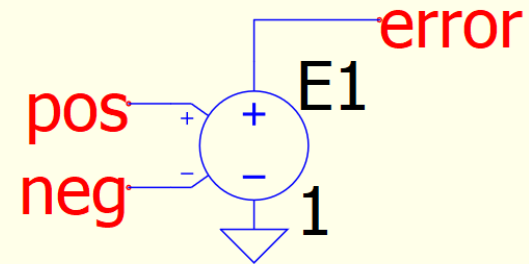


# PID Controller and Signal Limiter

Qspice : PID.qsym / Signal\_Limiter.qsym




- PID Controller

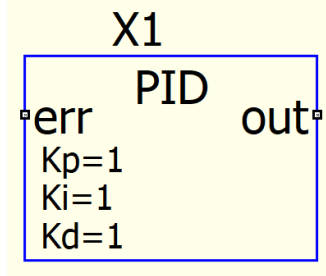- $$V_{out} = K_p V_{error} + K_i \int V_{error} dt + K_d \frac{dV_{error}}{dt}$$





- Signal Limiter

- limit(x,y,z) | intermediate value of x, y, and z, equivalent to min(max(x,y),z)

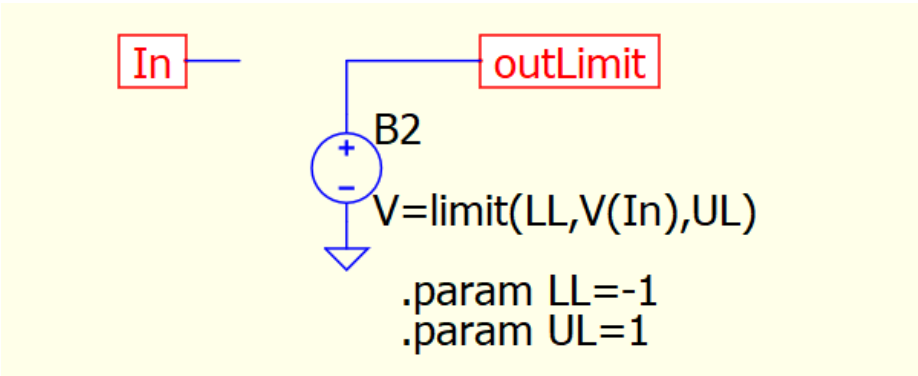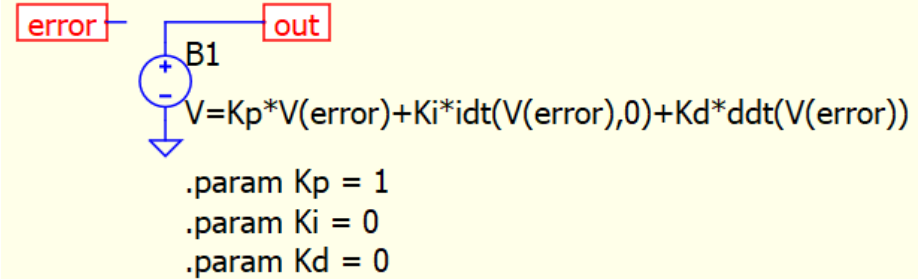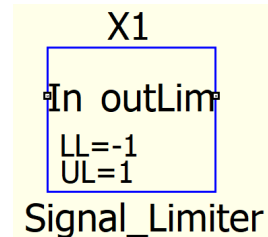

# Control System Symbol : Transient Simulation Example

Parent - PID CloseLoop (.tran).qsch

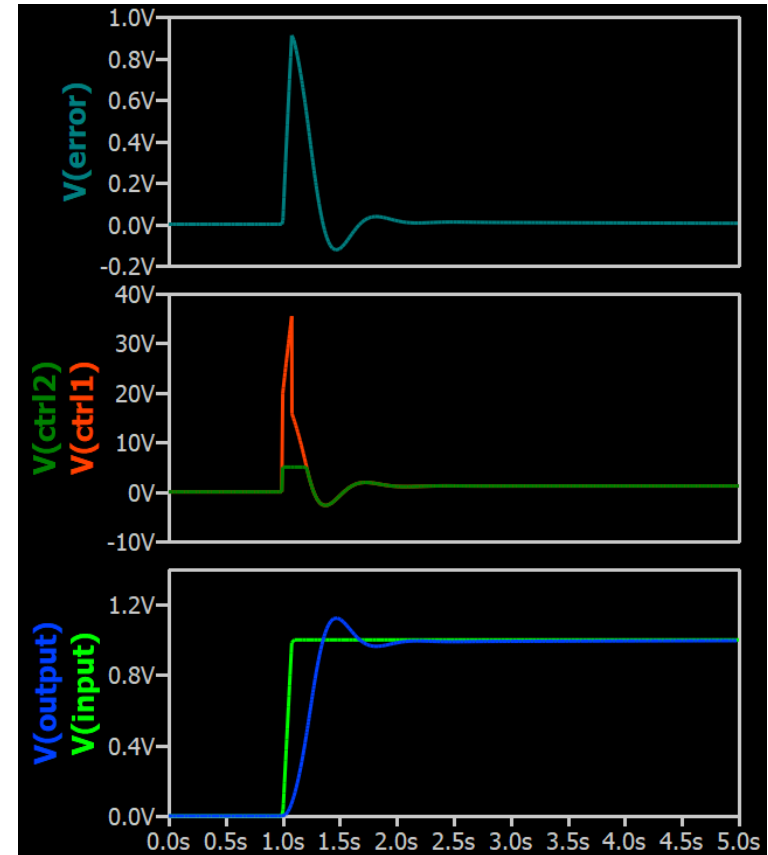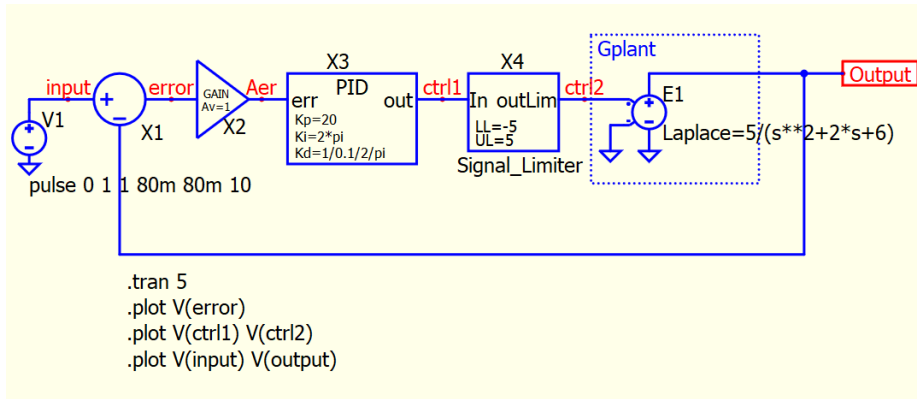

General Purpose

# Delay

## Qspice : Delay.qsym

- Delay

- Reason for Implementation


- Qspice B-source not offers delay function before 09/22/2023, but after that, Mike Engelhardt implemented delay(input,time) for arbitrary behavioral sources.

- Concept of Design



- T1 :  $T_d$  (delay) in ideal transmission line determines signal delay time
- R1 : To prevent signal reflection, transmission line must terminate with  $Z_0$
- B1 : To prevent loading effect when using delay block

- Symbol of delay.qsym

X1

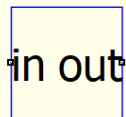

Tdelay=1m

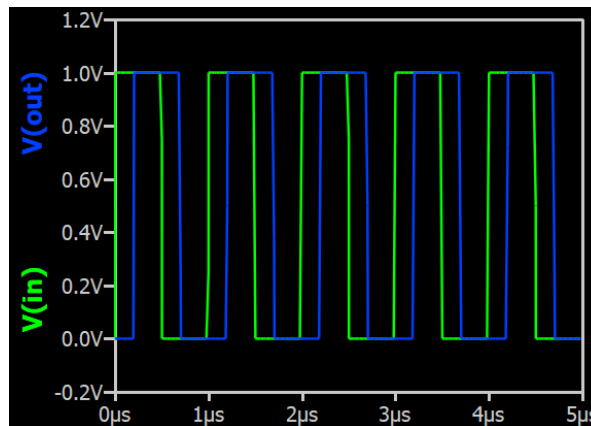
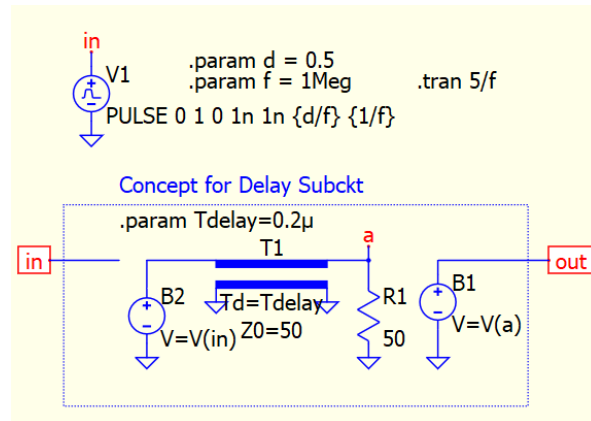


# SrcXXX Special Voltage Source and Potentiometer

Qspice : Scrxxxx.qsym / Potentiometer.qsym
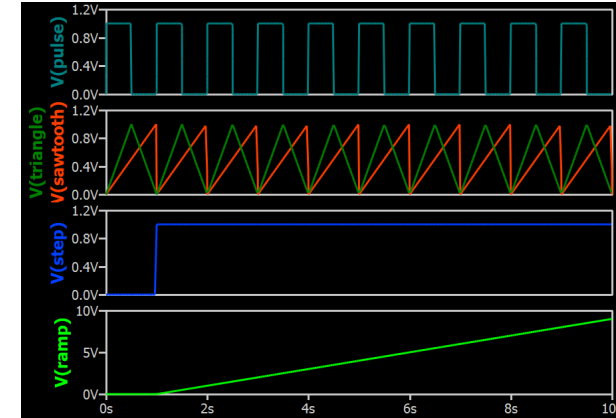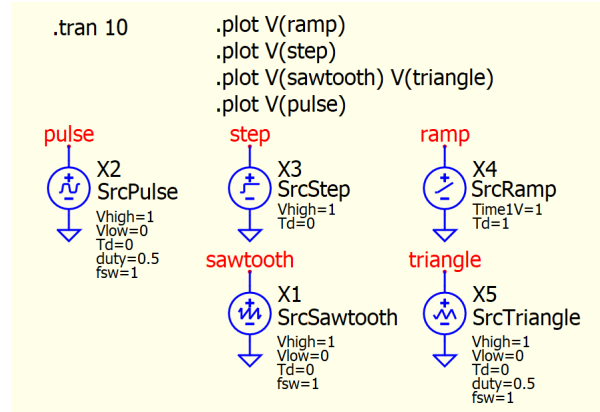
## • SrcXXX



- SrcPulse.qsym
- SrcSawtooth.qsym
- SrcTriangle.qsym
- SrcStep.qsym
- SrcRamp.qsym


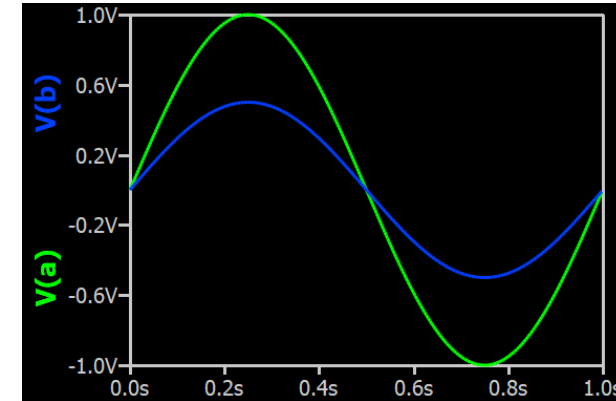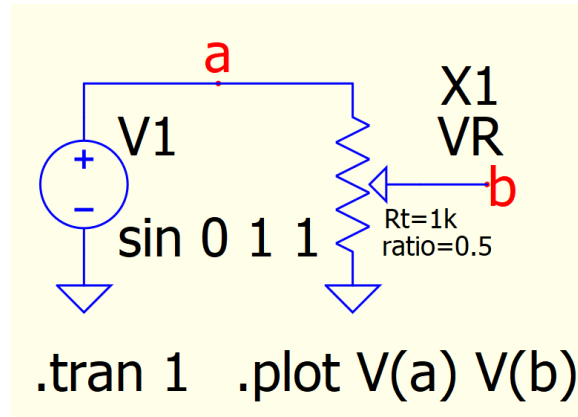
## • Potentiometer

- Symbol : Potentiometer.qsym
- Ratio is limited to [1m,0.999]
- Sub-circuit script

```
.subckt VR + - m params: Rt=1k ratio=0.5
.param w = limit(1m,ratio,0.999)
R1 + m (1-w)*Rt
R2 m - (w)*Rt
.ends VR
```



Special Subckt



# Voltage Control Current Source with Current Limit

Qspice : VCCS\_Ilimit.qsym

- VCCS\_Ilimit

- Use Behavioral source with  $\text{limit}(x,y,z)$  function


- Intermediate value of  $x$ ,  $y$ , and  $z$

- Sub-circuit

```
.subckt VCCS_Ilimit v+ v- out+ out-  
B1 out- out+ I=limit(gm*(V(v+)-V(v-)),Imax,Imin)  
.ends VCCS_Ilimit
```


- Symbols

X1  
VCCS\_ILIMIT1

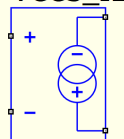


gm=1  
Imin=-1  
Imax=1

X2  
VCCS\_ILIMIT2


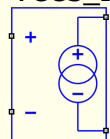


gm=1  
Imin=-1  
Imax=1

## Idea of VVCS with Current Limit

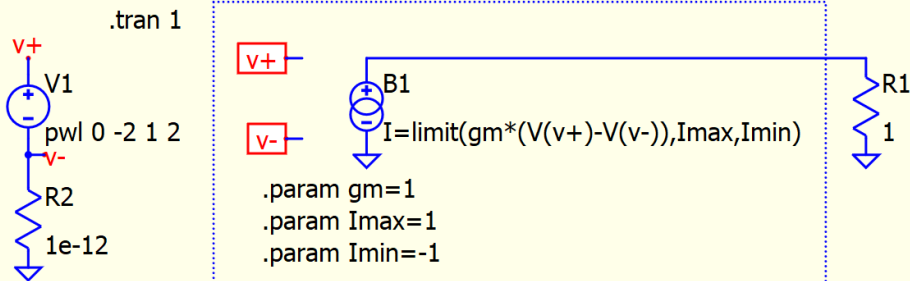

## Example

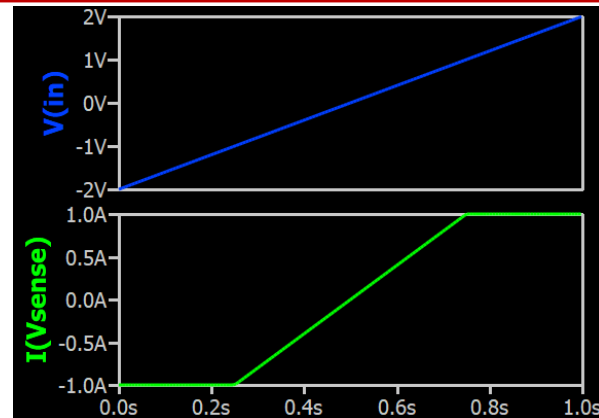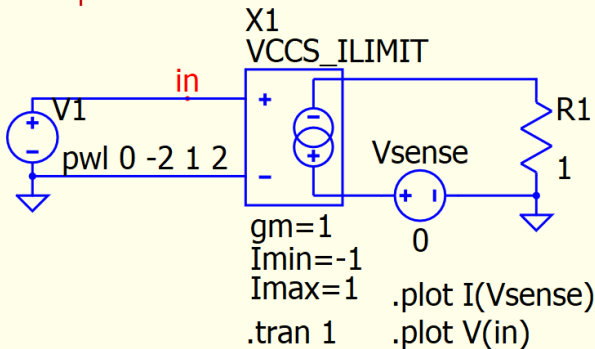

# Phase Shift Pulse with Delay Control

Qspice : PhaseShift\_KSK1.qsym

- PhaseShift\_KSK1.qsym
  - Use behavioral source with delay function to generate phase controlled pulse source
  - User to define switching frequency and duty as input parameters (these cannot be change during simulation)
  - Phase\_setpt is input port which control delay time in delay(), the delay is controlled with formula  $\frac{v_{phase\_setpt}}{2f_{sw}}$
  - A  $\frac{1}{f_{sw}}$  is used to prevent negative y value into delay(x,y,z)
  - z set to  $2f_{sw}$  to reduce waveform memory in simulation

Ideal of PhaseShift\_KSK1 subckt

